




Final Exam Study buide

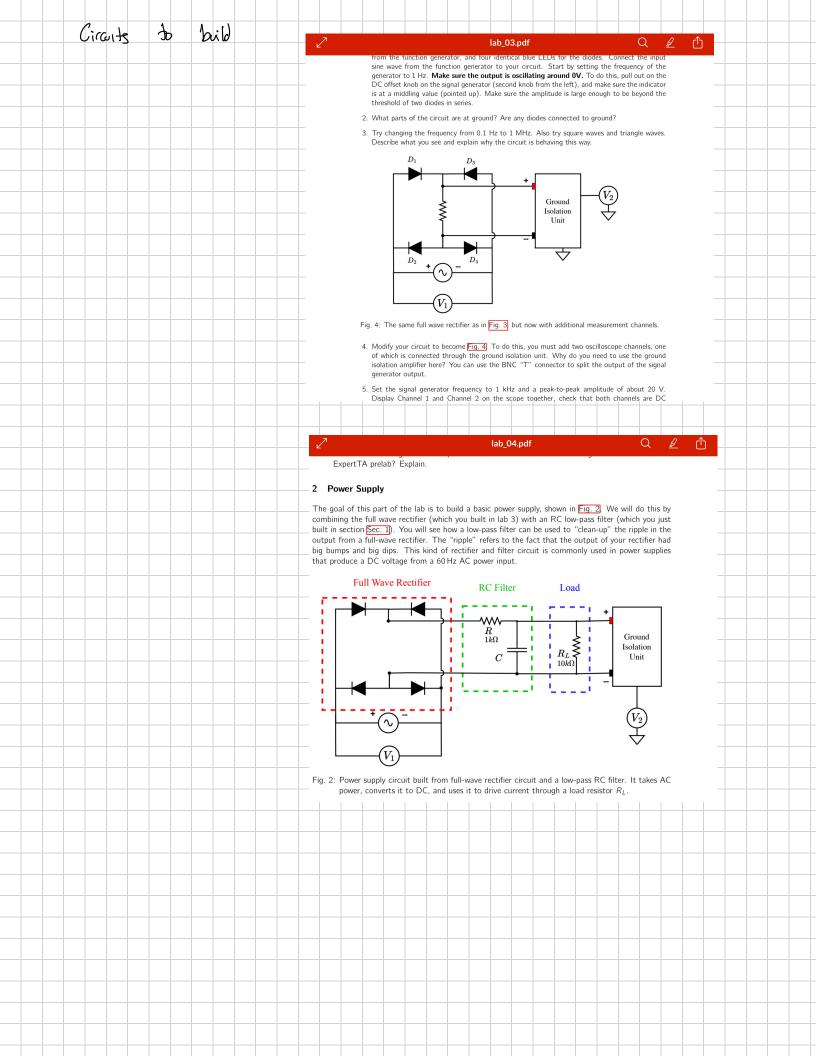


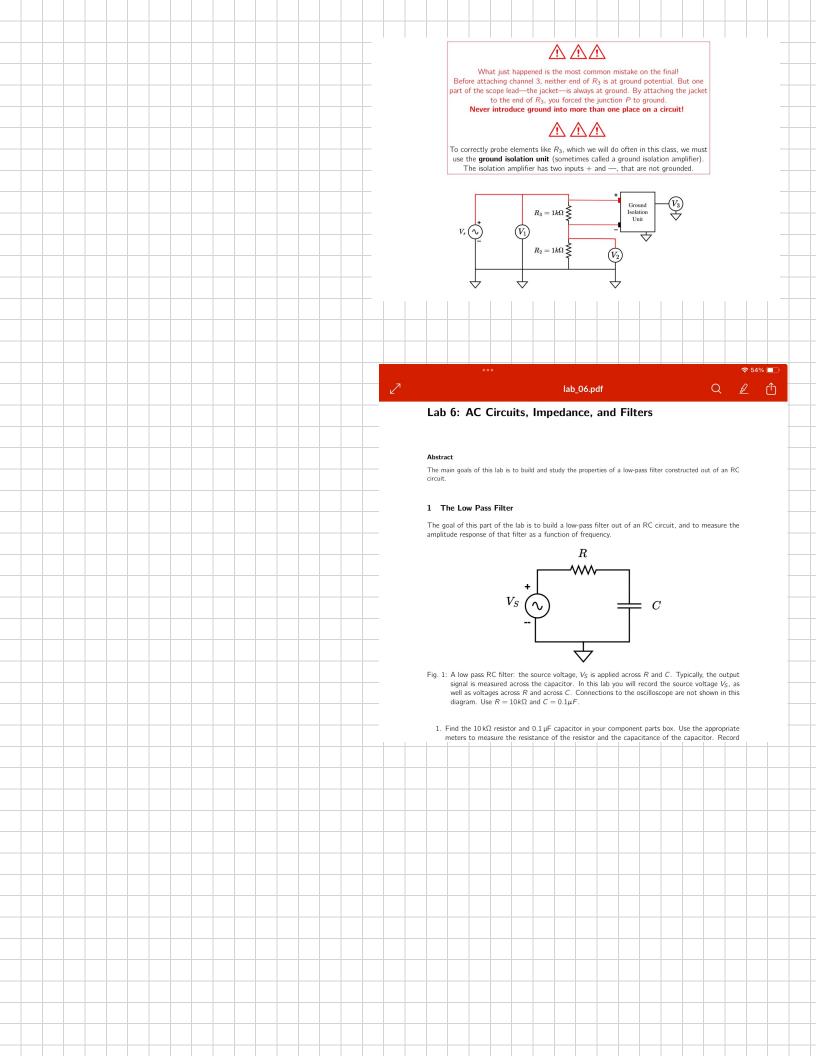

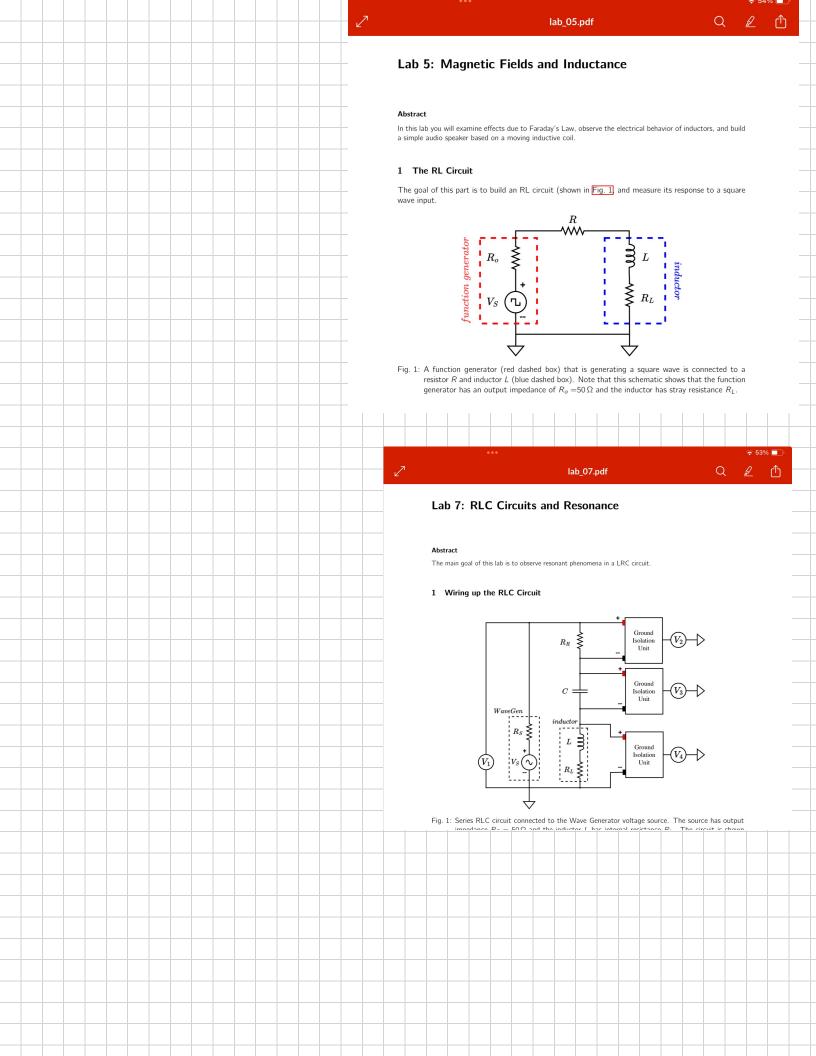

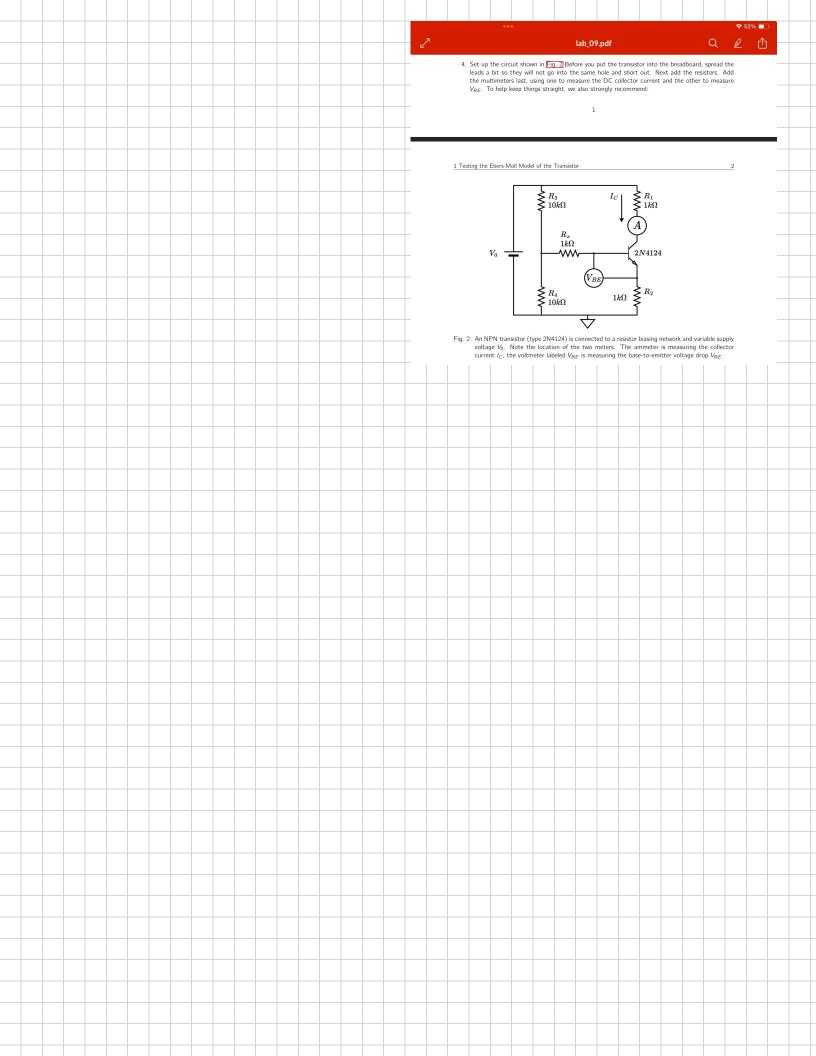

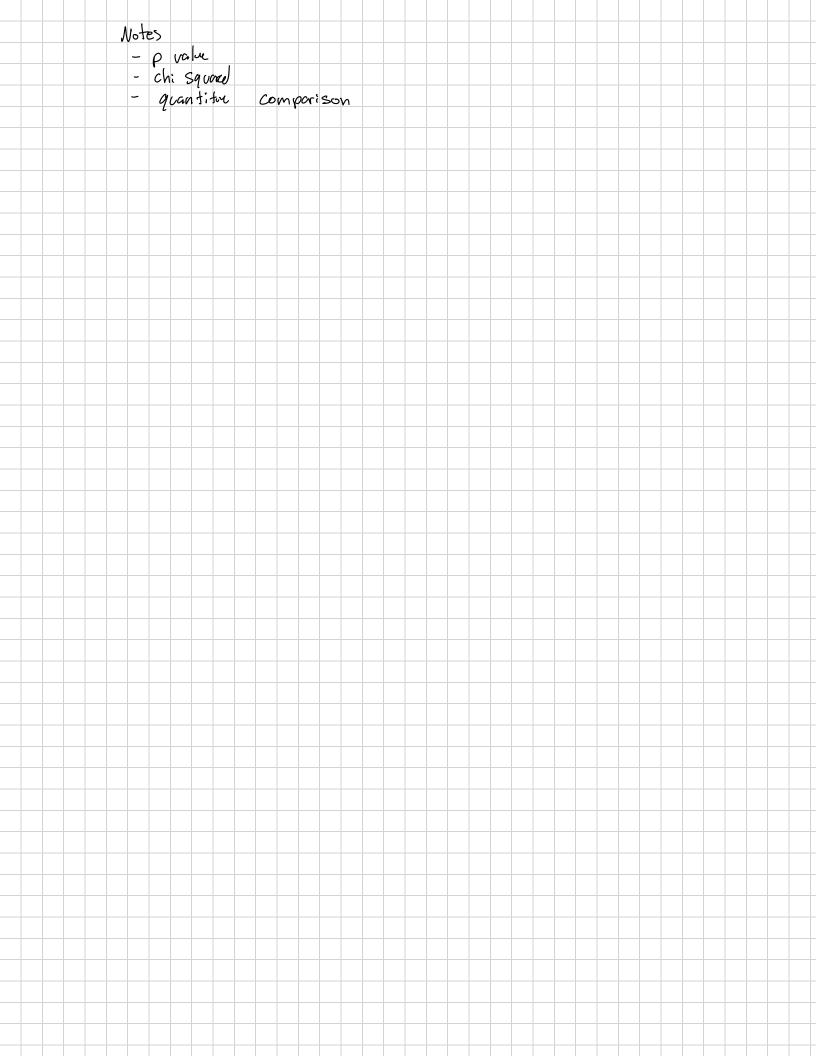

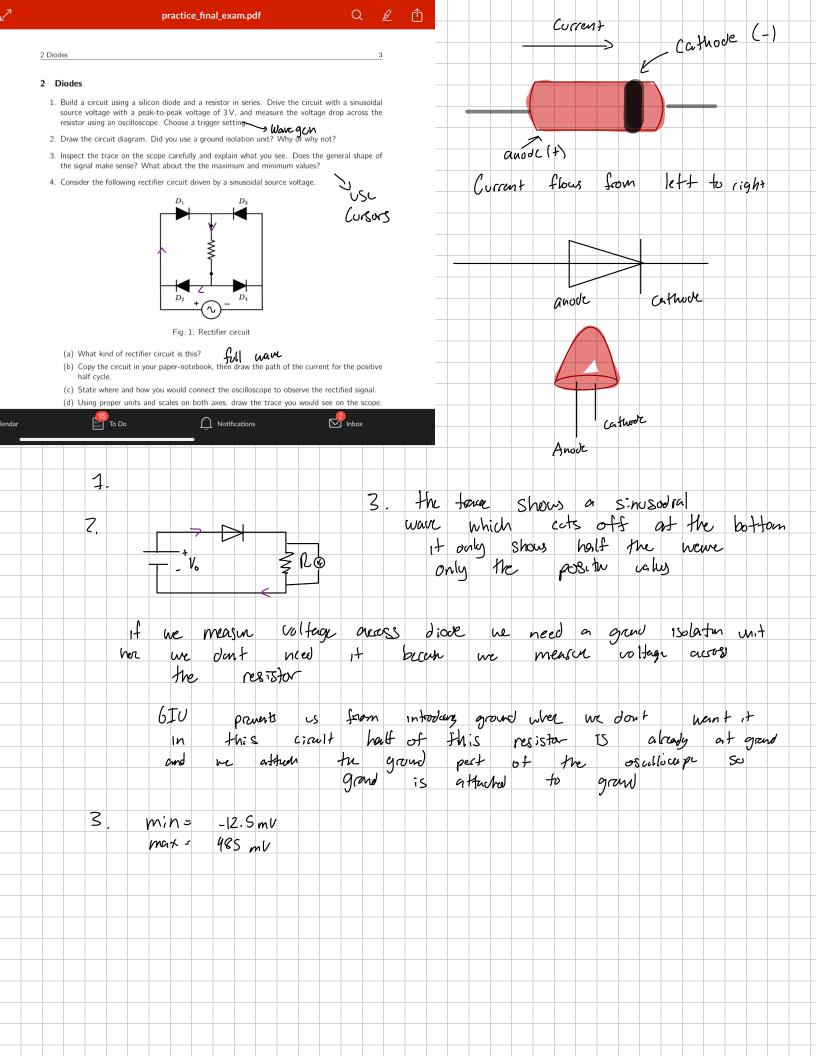


3 LR circuit:

4

3 LR circuit:

In your parts box find two resistors with resistance of approximately 10 $k\Omega$ and an inductor with inductance $L=100\,\mathrm{mH}$.

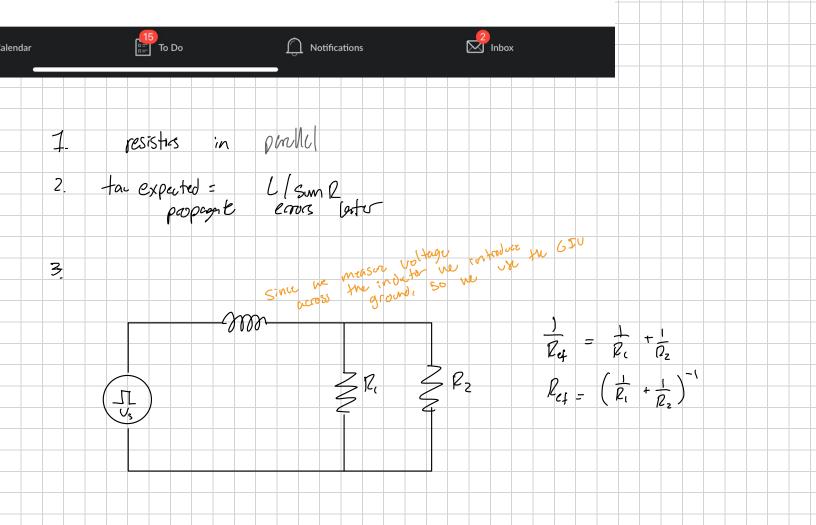- 1. How would you connect these elements so that your circuit has a characteristic time constant of $20\,\mu s$?
- 2. Measure the values of the resistance and the inductance, calculate the expected time constant τ with the parts you have, and propagate uncertainties to determine the uncertainty in the expected value of τ .
- 3. Draw your circuit that shows the resistor combination and the inductor in series with a square wave source. Build the circuit and drive it with a positive square wave between 0 V and 5 V. Set up your scope to measure the voltages across the resistors and across the inductor. Think about whether you need to use a ground isolation unit. Display these traces together with the source voltage on your scope.
- 4. Transfer the traces to the computer and analyze the data to extract the time constant, τ , of your circuit using a linear fit.
- 5. You must also determine the uncertainty in τ and evaluate the goodness of your fit. To simplify data acquisition, you may consider that the uncertainty for all voltage values is 3%. State your reduced χ^2 value and the P-value for your comparison between data and fit.
- 6. Quantitatively compare your calculated and measured values of tau. Do your calculation on paper, and use the notebook only to compute numerical values.



LRC circuit 1. Choose a resistor, an inductor and a capacitor from your parts box and measure their resistance, inductance and capacitance, respectively. 2. Use these values to predict the resonance frequency and the quality factor of your circuit. Be sure to propagate uncertainties as needed. Don't forget about the 50Ω in the source, as well as the internal resistance of the inductor. 3. Draw the circuit diagram for an RLC circuit using these parts and a sine wave generator. 4. Imagine you drove the system at resonance. Sketch a plot of what you expect the voltage across the resistor, inductor, and capacitor to look like. Pay attention to the relative magnitudes and phases. 5. Now, build your RLC circuit with these elements using the function generator as your source. Choose a sine-wave as source, and set the peak-to-peak voltage of your source to 1 V. Measure the voltages across all three circuit elements and display them together with your source voltage on the screen of the oscilloscope. 6. Tune the frequency of the source signal to resonance. In your notebook, comment on the relative phase shifts between the four signals displayed. Do they agree with your prediction above? 7. Determine the quality factor of the circuit from the traces displayed. 8. Compare the measured quality factor with the predicted one. Do they agree? You must give a quantitative answer. 9. Review the resonance curve that you measured in Lab 7 (voltages vs frequency) and explain why the curves for V_C and V_L are asymmetric. Be sure to understand how the capacitor and the inductor behave below and above resonance.